

EXPERIMENT-1


AIM:

To find the equivalent resistance using series parallel reduction.

PROCEDURE:

SERIES AND PARALLEL REDUCTION

CIRCUIT DIAGRAM

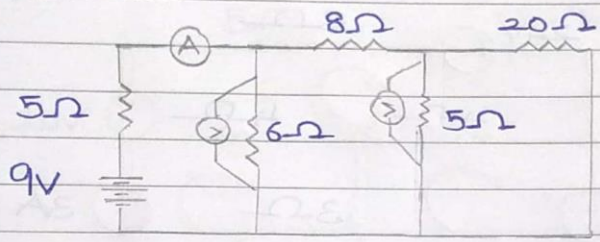

FIND THE CURRENT FLOWING THROUGH THE CIRCUIT

20Ω and 5Ω are in parallel connection

$$R_{eq1} = \frac{20 \times 5}{20 + 5} = 4\Omega$$

R_{eq1} and 8Ω are in series connection

$$R_{eq2} = 4 + 8 = 12\Omega$$

R_{eq2} and 6Ω are in parallel connection

$$R_{eq3} = \frac{12 \times 6}{12 + 6} = 4\Omega$$


R_{eq3} and 5Ω are in series connection

$$R_{eq} = 4 + 5 = 9\Omega$$

$V = IR \Rightarrow I = \frac{V}{R}$

$$I = \frac{9V}{9\Omega} = 1A$$

MULTISIM:

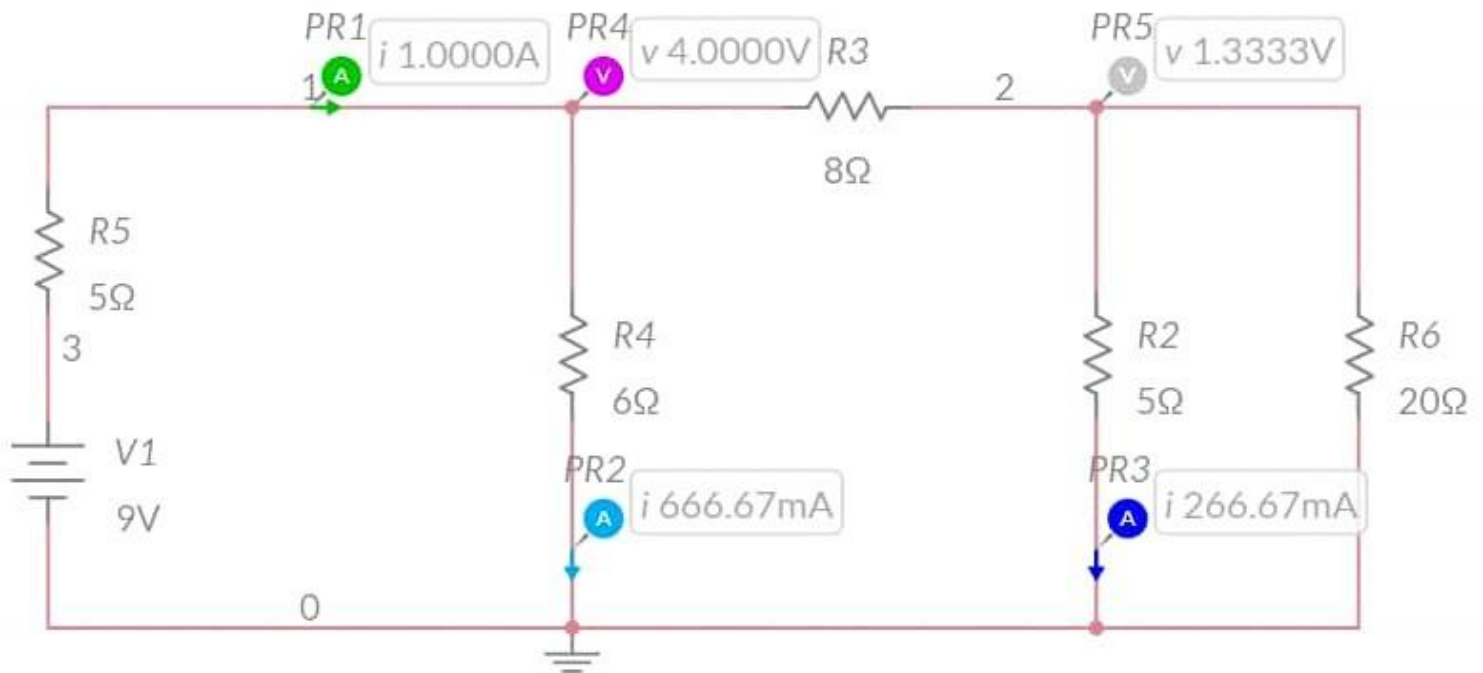

CONCLUSION:

The current value calculated theoretically and through MULTISIM are the same. Therefore, the equivalent resistance calculated theoretically is correct.

Effective current value=1A & effective resistance value=9ohms

NAME: G R NITIN

ROLL NO: CB.EN.U4CYS21017