

Computer Arithmetic

Logic Gates

- The electronics inside a modern computer are digital.
- Digital electronics operate with only two voltage levels of interest: a high voltage and a low voltage.
- *A logic gate is a simple switching circuit that determines whether an input pulse can pass through to the output in digital circuits.*
- Logic gates use Boolean algebra to execute logical processes.
- Logic gates are found in nearly every digital gadget we use on a regular basis. Logic gates are used in the architecture of our telephones, laptops, tablets, and memory devices.

- Logic blocks are categorized as one of two types, depending on whether they contain memory.
- Blocks without memory are called **combinational**; the output of a combinational block depends only on the current input.
- In blocks with memory called the **Sequential**, the outputs can depend on both the inputs and the value stored in memory, which is called the state of the logic block.
- **Combinational logic**: A logic system whose blocks do not contain memory and hence compute the same output given the same input.
- **Sequential logic**: A group of logic elements that contain memory and hence whose value depends on the inputs as well as the current contents of the memory

Boolean Algebra

- *Boolean algebra is a type of logical algebra in which symbols represent logic levels.*
- *The digits(or symbols) 1 and 0 are related to the logic levels in this algebra; in electrical circuits, logic 1 will represent a closed switch, a high voltage, or a device's "on" state. An open switch, low voltage, or "off" state of the device will be represented by logic 0.*
- A light bulb can be used to demonstrate the operation of a logic gate. When logic 0 is supplied to the switch, it is turned off, and the bulb does not light up. The switch is in an ON state when logic 1 is applied, and the bulb would light up. In integrated circuits (IC), logic gates are widely employed.




Truth table

- *The outputs for all conceivable combinations of inputs that may be applied to a logic gate or circuit are listed in a truth table. When we enter values into a truth table, we usually express them as 1 or 0, with 1 denoting True logic and 0 denoting False logic.*




Types of Logic gates

- A logic gate is a digital gate that allows data to be transferred. Logic gates, use logic to determine whether or not to pass a signal. Logic gates, on the other hand, govern the flow of information based on a set of rules. The following types of logic gates are commonly used:
 - AND
 - OR
 - NOT
 - NOR
 - NAND
 - XOR
 - XNOR

Digital Logic Gate Symbols

GATE	SYMBOL	NOTATION	TRUTH TABLE																		
<u>AND</u>		$A \cdot B$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>A AND B</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	INPUT		OUTPUT	A	B	A AND B	0	0	0	0	1	0	1	0	0	1	1	1
INPUT		OUTPUT																			
A	B	A AND B																			
0	0	0																			
0	1	0																			
1	0	0																			
1	1	1																			
<u>OR</u>		$A + B$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>A OR B</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	INPUT		OUTPUT	A	B	A OR B	0	0	0	0	1	1	1	0	1	1	1	1
INPUT		OUTPUT																			
A	B	A OR B																			
0	0	0																			
0	1	1																			
1	0	1																			
1	1	1																			
<u>NOT</u>		\overline{A}	<table><tr><th>INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>NOT A</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	INPUT	OUTPUT	A	NOT A	0	1	1	0										
INPUT	OUTPUT																				
A	NOT A																				
0	1																				
1	0																				


inverter

<u>NAND</u>		$\overline{A \cdot B}$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>A NAND B</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	INPUT		OUTPUT	A	B	A NAND B	0	0	1	0	1	1	1	0	1	1	1	0
INPUT		OUTPUT																			
A	B	A NAND B																			
0	0	1																			
0	1	1																			
1	0	1																			
1	1	0																			
<u>NOR</u>		$\overline{A + B}$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>A NOR B</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	INPUT		OUTPUT	A	B	A NOR B	0	0	1	0	1	0	1	0	0	1	1	0
INPUT		OUTPUT																			
A	B	A NOR B																			
0	0	1																			
0	1	0																			
1	0	0																			
1	1	0																			
<u>XOR</u>		$A \oplus B$	<table><tr><th colspan="2">INPUT</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>A XOR B</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	INPUT		OUTPUT	A	B	A XOR B	0	0	0	0	1	1	1	0	1	1	1	0
INPUT		OUTPUT																			
A	B	A XOR B																			
0	0	0																			
0	1	1																			
1	0	1																			
1	1	0																			


$$\overline{A}B + A\overline{B}$$

- Buffer gate :

 A buffer, is a **basic logic gate that passes its input, unchanged, to its output**. Its behavior is the opposite of a NOT gate. The main purpose of a buffer is to regenerate the input, usually using a strong high and a strong low



Input	Output
0	0
1	1

 

Representing Boolean expressions as circuits:


- Minimizing the expression
- Representing using gates

PROPERTIES OF BOOLEAN ALGEBRA:

- Identity law: $A + 0 = A$ and $A \cdot 1 = A$
- Zero and One laws: $A + 1 = 1$ and $A \cdot 0 = 0$
- Inverse laws: $A + \bar{A} = 1$ and $A \cdot \bar{A} = 0$
- Commutative laws: $A + B = B + A$ and $A \cdot B = B \cdot A$
- Associative laws: $A + (B + C) = (A + B) + C$ and $A \cdot (B \cdot C) = (A \cdot B) \cdot C$
- Distributive laws: $A \cdot (B + C) = (A \cdot B) + (A \cdot C)$ and $A + (B \cdot C) = (A + B) \cdot (A + C)$


$\overline{1} \quad \overline{y}, y'$

 - The function (a) $F = x'y'z + x'yz + xy'$ can be minimized to (b) $F = x'z + xy'$



 (a) $F2 = x'y'z + x'yz + xy'$

$$\begin{aligned}
 & x'y'z + x'yz + xy' \\
 & x'z(y' + y) + xy' \\
 & x'z(1) + xy'
 \end{aligned}$$




(b) $F2 = xy' + x'z$

Arithmetic for Computers

- Operation on integers
 - Addition and Subtraction
 - Multiplication and Division
 - Dealing with overflow
- Floating point real numbers
 - Representation and operations

- Example = 7+6

 

- Overflow if result out of range
 - Adding +ve and -ve operands, no overflow
 - Adding two +ve operands
 - overflow if sign bit is 1 (answer comes negative)
 - Adding two -ve operands
 - overflow if sign bit is 0 (answer comes positive)

- **Overflow:**

- In computer architecture 2's Complement Number System is widely used.

- N-bit 2's Complement number System can represent Number from -2^{n-1} to $2^{n-1} - 1$

- 4 Bit can represent numbers from (-8 to 7)

- 5 Bit can represent numbers from (-16 to 15) in 2's Complimentary System.

- Overflow Occurs with respect to addition when 2 N-bit 2's Complement Numbers are added and the answer is too large to fit into that N-bit Group.

- A computer has N-Bit Fixed registers. Addition of two N-Bit Number will result in a max N+1 Bit number. That Extra Bit is stored in carry Flag. But Carry does not always indicate overflow.

- Adding $7 + 1$ in 4-Bit must be equal to 8. But 8 cannot be represented with 4 bit 2's complement number as it is out of range. Two Positive numbers were added and the answer we got is negative (-8). Here Carry is also 0. It is normally left to the programmer to detect overflow and deal with this situation.

Adding $7 + 1$ In 2's Compliment

$$\begin{array}{rcccccl}
 & 0 & 0 & 0 & 1 & (1) \\
 + & 0 & 1 & 1 & 1 & (7) \\
 \hline
 & 1 & 0 & 0 & 0 & (-8)
 \end{array}$$

- **Overflow Detection –**
Overflow occurs when:
 - Two negative numbers are added and an answer comes positive or
 - Two positive numbers are added and an answer comes as negative.